

BATCH 11 - Smart Home Voice Controlled Automation

by

Saranish R – 727723eucs212

Saravanan C – 727723eucs214

Rudhresh - 727723eucs196

Santhosh – 727723eucs208

Components Used in Smart Home Voice Controlled Automation

Components Needed:

1. **NodeMCU ESP8266** (3.3V logic)
2. **5V Relay Module** (Opto-isolated preferred for safety)
3. **AC Bulb & Holder**
4. **Jumper Wires** (Female-to-Female recommended)
6. **5V Power Supply** (for relay, can be USB or external)
7. **AC Power Cord** (with live & neutral wires)

Wiring Connections:

1. NodeMCU to Relay:

NodeMCU Pin	Relay Pin
-----	-----
3.3V	VCC
GND	GND
D1 (GPIO5)	IN

2. Relay to AC Bulb:

- AC Live (L) → COM (Common on relay)
- NO (Normally Open) → Bulb Live Wire
- Bulb Neutral (N) → AC Neutral (Direct)